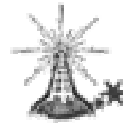


# Introduction to EMI filter Design

---

Presented by : Vuttipon Tarateeraseth



1



## What're EMI filters ?

---

- EMI filter is specifically named of “filter circuits” that used to reduce the “EMI” generated by power electronics equipments.
- The EMI filter can't be used to filter out mains harmonics.


2

## Why should be EMI filter ?


- “EMI Filter” is an important mitigation equipment for suppressing undesired conducted electromagnetic interference (EMI )

3

## Where're EMI filters ?

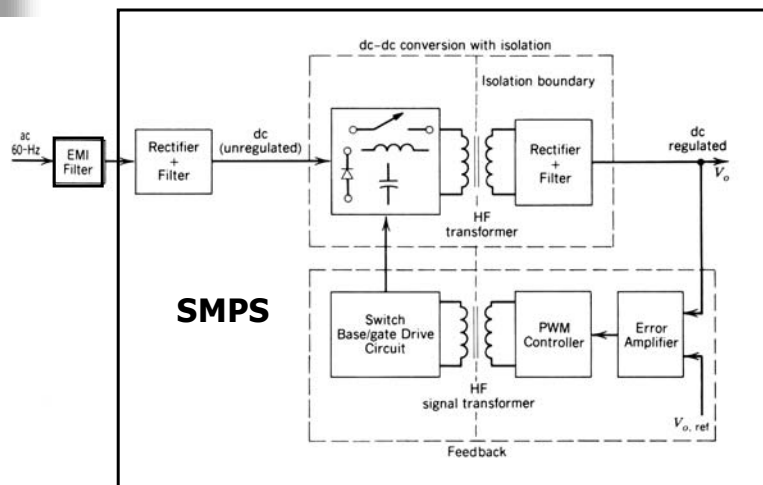


4

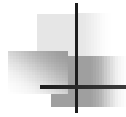

## Eyes of EMI filter designers


- **EMI filter designers** thinks in terms of attenuation, insertion loss, voltage drop and the number of filter sections required to meet the insertion loss
- **True filter houses** speak of poles, zeros, group delay, predistortion, attenuation and the order of the filter

5

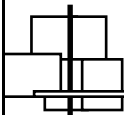

## Basic concepts

6

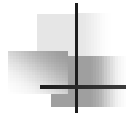


## Basic concepts

---

- Insertion Loss
- Lump Element Low Pass Filters

7

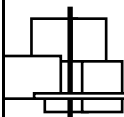

## Insertion Loss

---

8

## What's Insertion Loss ?

- The Insertion Loss (  $IL_{dB}$  ) gives the reduction in the load voltage at the frequency of interest due to the insertion of the filter

9

## What's Insertion Loss ? ( con't )

$$IL_{dB} = 20 \log_{10} \left[ \frac{V_{L,wo}}{V_{L,w}} \right]$$


$V_{L,wo}$  = The output voltage of the signal source without the filter being connected in the circuit

$V_{L,w}$  = The output voltage of the signal source at the output terminals of the filter with the filter in the circuit

( not transfer function )

10

## Insertion loss ( con't )

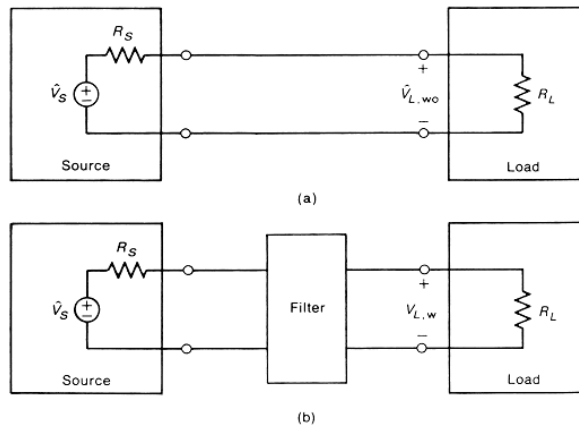

11

## Lump element Low Pass filters

12



## Lump Element Low-Pass Filters

- Filtering concept
- The simple capacitive filter
- The simple Inductive filter
- Cascade LC, T,  $\pi$  and Why should be cascaded ?
- EMI filter


13



## Filtering concepts


- Filters are designed to attenuate at certain frequencies while permitting energy at other frequencies to pass unchanged
- The role of a filter in attenuating by providing maximum mismatch impedance at undesired frequencies while providing maximum matching impedance at desired frequencies to pass unchanged

14

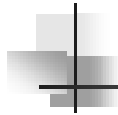


## Various signal filters

Figure 3A  
Different types of single-line filter

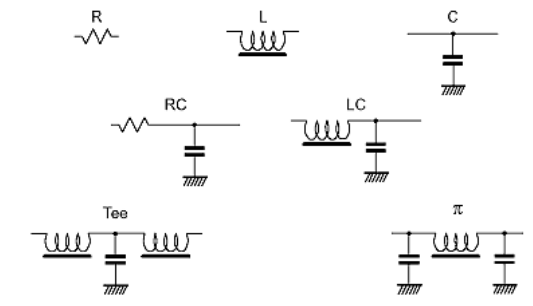


15

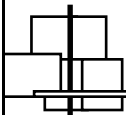

## Simple capacitive filter

16

## The simple capacitive filter

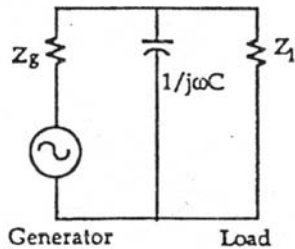

$$IL_{dB} = 20 \log_{10} \left| 1 + \frac{Z_p}{Z_c} \right|$$

$Z_p$  = The Impedance of the parallel combination of  $Z_g$  and  $Z_l$   
 $(Z_g * Z_l) / (Z_g + Z_l)$

$Z_c$  = The impedance of the filtering capacitor,  
 $1/j\omega C$

17

## The simple capacitive filter ( con't )

- Capacitive is effective as a filter when

$$Z_c \ll Z_p$$

Therefore, Source and Load impedance connected with capacitor should be **high impedance**

- Insertion level** = 20dB/decade  
 = 6 dB/octave

18

## The simple capacitive filter ( con't )

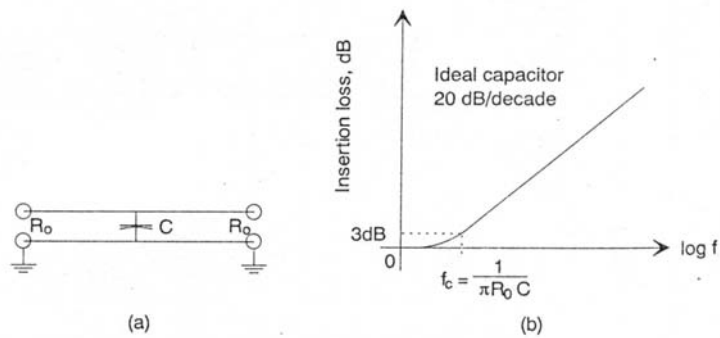


Figure 10-3 Capacitor filter and its response characteristics

19

## The simple capacitive filter ( con't )

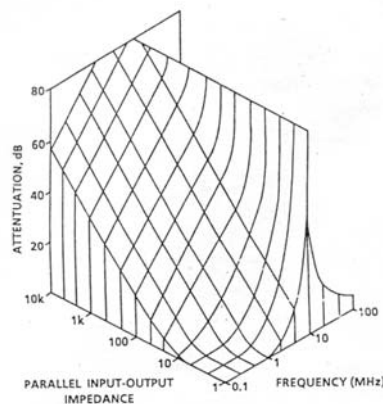



Figure 2-4. Capacitor attenuation versus frequency and  $Z_p$ . (Copyright © 1991, EMC Services. All rights reserved. Printed with permission.)

20

## Simple inductive filter

21

## The simple inductive filter

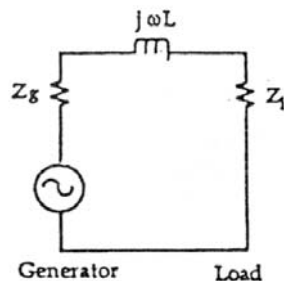

$$IL_{dB} = (20) \log_{10} \left| 1 + \frac{Z_{ind}}{Z_{sum}} \right|$$

$Z_{sum}$  = The Impedance of the series combination of  $Z_g$  and  $Z_l$ , ( $Z_g + Z_l$ )

$Z_{ind}$  = The impedance of the filtering inductor,  $j\omega L$

22

## The simple Inductive filter ( con't )

- Inductive is effective as a filter when


$$Z_{ind} \gg Z_{sum}$$

Therefore, Source and Load impedance connected with inductor should be **low impedance**


- Insertion level = 20dB/decade  
= 6 dB/octave

23


## The simple Inductive filter ( con't )

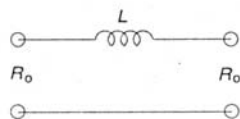

(a)

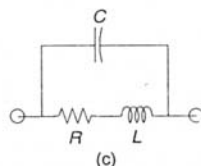

(c)

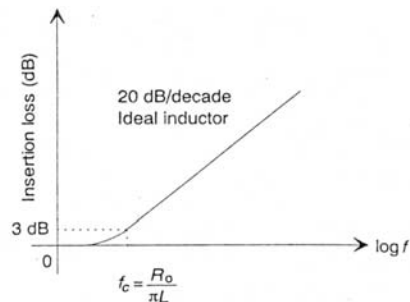

(b)

**C** = parasitic capacitance  
**R** = parasitic resistance

Figure 10-5 Inductor filter

24

## The simple Inductive filter ( con't )

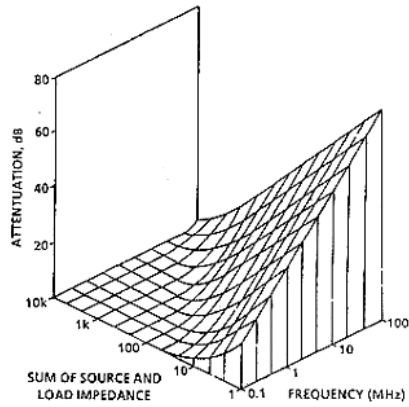


Figure 2-7. Inductor attenuation versus frequency and  $Z_{sum}$ . (Copyright © 1991, EMC Services. All rights reserved. Printed with permission.)

25

## Cascade filter

26

## Cascade LC, T, $\pi$ and Why should be cascaded ?

- **How should you do ?** if  $Z_{in}$  and  $Z_{out}$  is dissimilar ,for example :  $Z_{in} = \text{high}$  ,  $Z_{out} = \text{low}$  or vice versa, or when you want to increase the Insertion Loss !!

**Ans** Cascade LC, T and  $\pi$  filters are mostly useful when the source and load impedances are very dissimilar or when you want to increase the insertion loss!!!

27

## LC filter

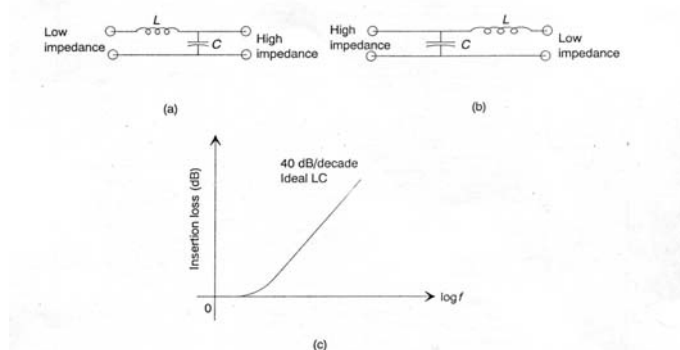


Figure 10-6 (a) L-section for low source impedance and high load impedance (b) L-section for high source impedance and low load impedance (c) insertion-loss characteristics for equal impedance terminations

28

## π - filter

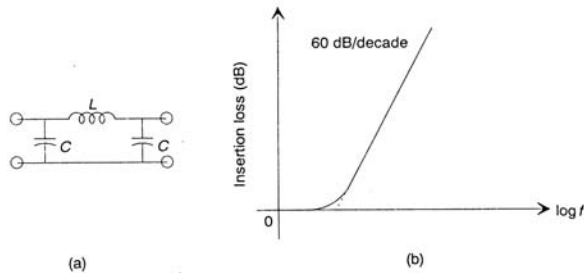


Figure 10-7  $\pi$ -section filter

**10-2-2-4  $\pi$ -Section Filter.** This configuration, which is shown in Figure 10-7(a), is the most common type used in practice. Its advantages include an ease of manufacture, higher insertion loss over a broad frequency band, and moderate space requirements.

When  $Z_g = Z_L = R_0$ , the insertion loss [4] is given by

## T – filter

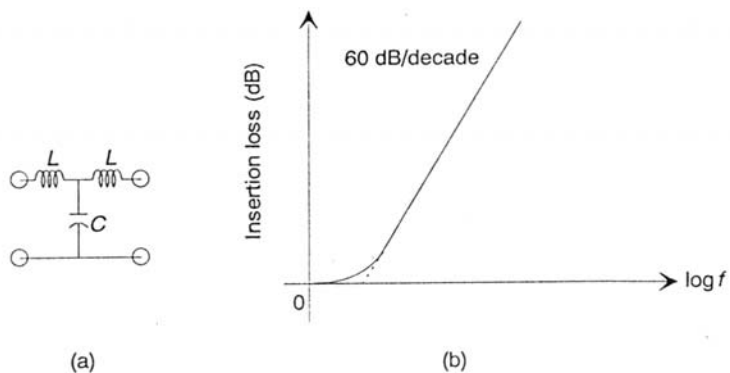


Figure 10-8 T-section low-pass filter

## Conclusion for effective filtering

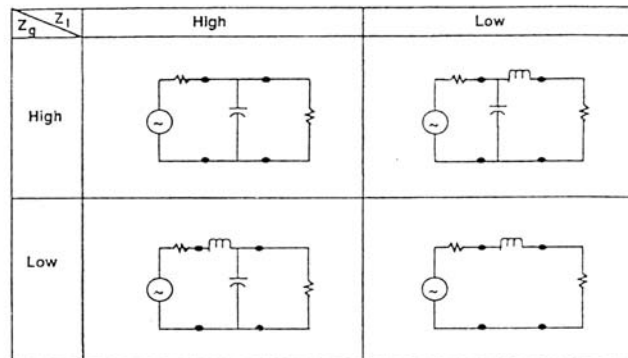


Figure 2-9. Filter selection matrix. (Copyright © 1991, EMC Services. All rights reserved. Printed with permission.)

31

## Conclusion for effective filtering ( con't )

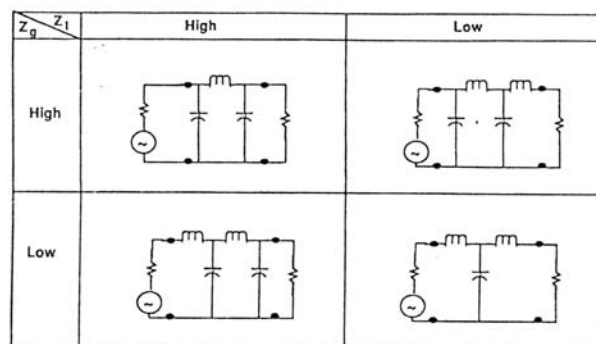


Figure 2-10. Higher order roll-off filter selection matrix. (Copyright © 1991, EMC Services. All rights reserved. Printed with permission.)

32


# EMI FILTER

33

## EMI filter
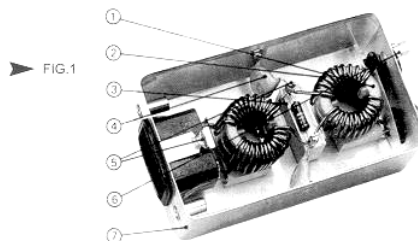
### Construction and Design

- Toroid cover for perfect insulation, with built-in spacers to maintain creepage distance between windings. ①
- Precision balance of inductance between windings to prevent core saturation at full load. ②
- Only capacitors that comply with VDE 0565-1 are used. ③
- Low leakage current. ④
- Both crimped and soldered connections. ⑤
- Anti-rotation terminals to prevent open connections. ⑥
- Corrosion-proof case. ⑦



34

# Main Idea !!!



- **Diagnosing conducted EMI noise mode**

Two conducted noise modes :

Differential Mode (DM) and Common Mode (CM),


**Dealt with separately in EMI filter design**

- **Methods:**


- ⊗ Differential mode rejection network
- ⊗ Current probe
- ⊗ Noise separator

35


## A basic of EMI filter diagram

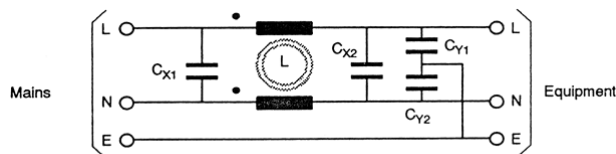

Equivalent circuit for differential mode

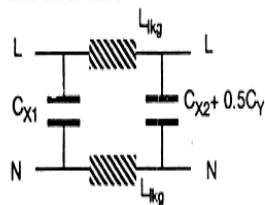


Equivalent circuit for common mode

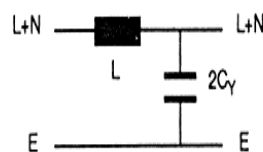


36

## Common mode choke

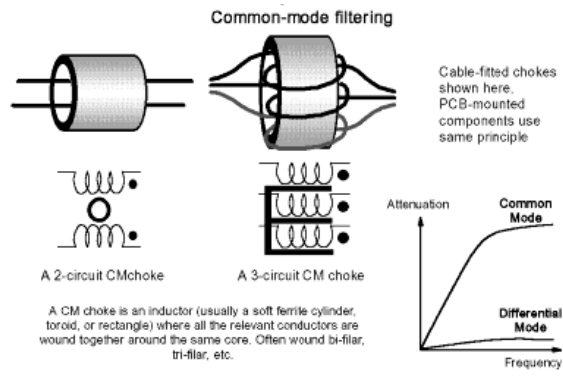


37
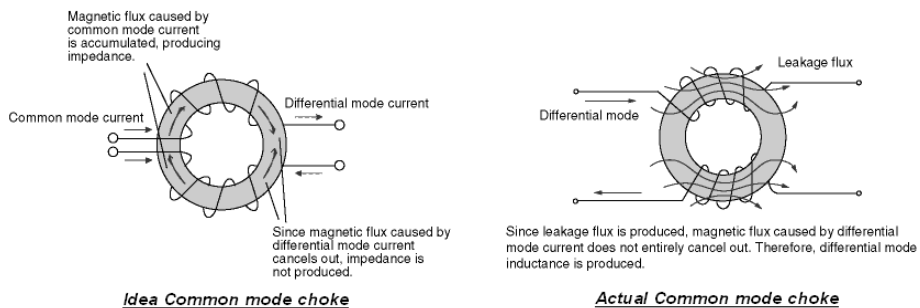
## Effect of the filter elements on Common and Differential mode currents



38
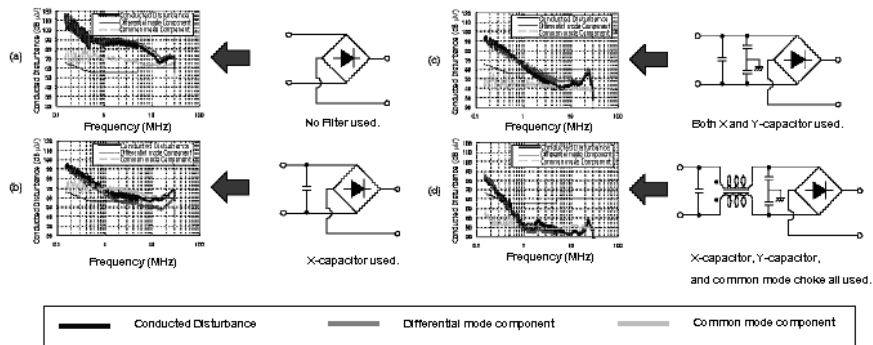
## Separation of the conducted Emissions into Common and Differential mode currents



39

## Higher performance mains EMI filters


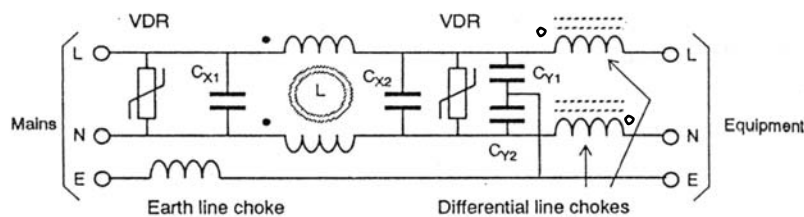


Figure 7.24 Higher performance mains filter


40

## Metal Oxide Varistors ( MOVs )

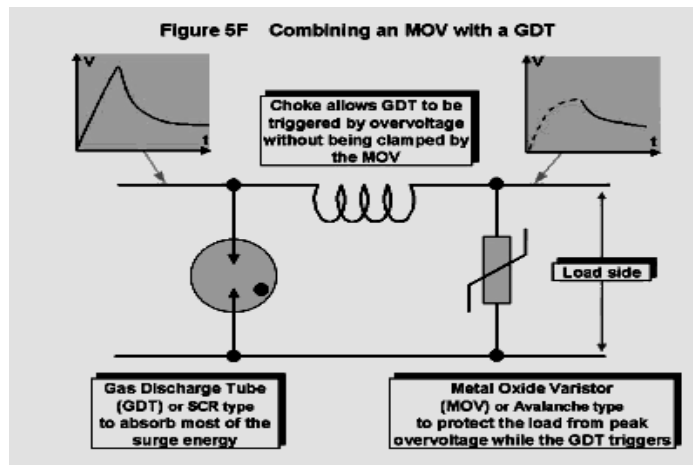


41

## Metal Oxide Varistors ( MOVs )

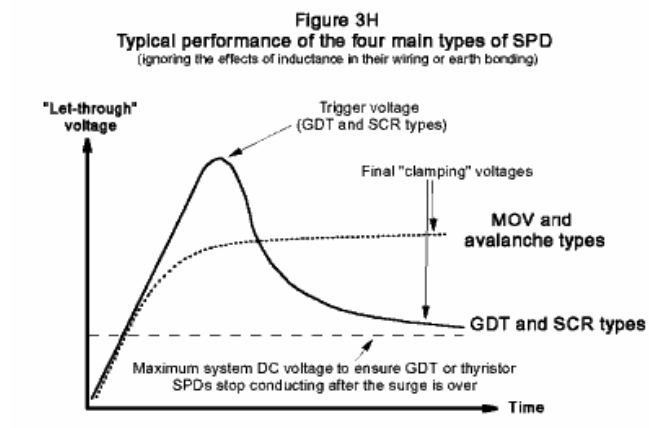

42

## EMI filter in SMPS

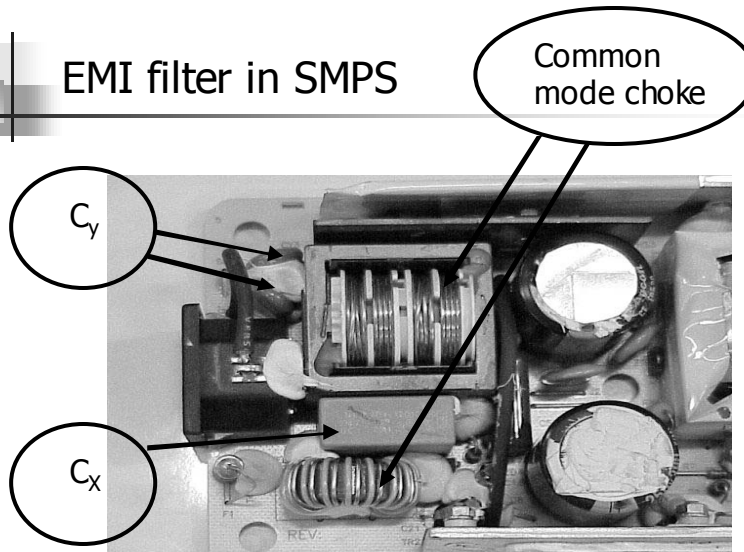


43

## Packaging of EMI filters



44

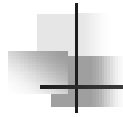

## References

---

- EMC for Product designers, Tim William
- EMI Filter Design, Richard Lee Ozenbaugh
- Engineering Electromagnetic Compatibility, V.Prasad Kodali
- Controlling conducted emissions by design, John C. Fluke. Sr.
- Power line filter design for switched-mode power supplies, Mark J. Nave
- Handbook of electromagnetic compatibility, edit by Reinaldo Perez